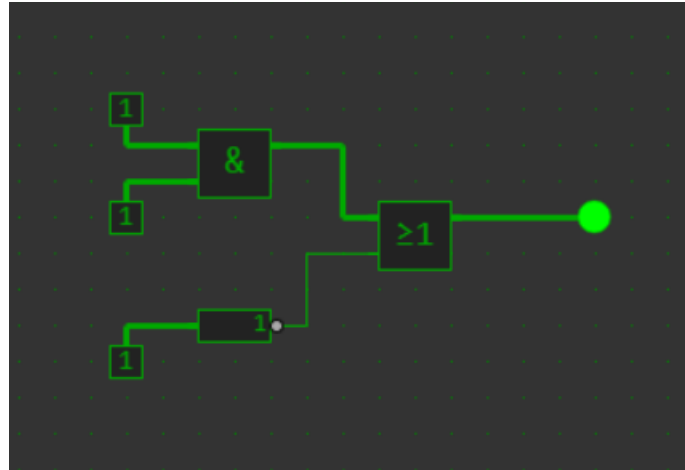


Tablas de Verdad


José Antonionio Alcántara Quintero Mármol

Circuito 1



p	q	p AND q	NOT q	(p AND q) OR (NOT q)
V	V	V	F	V
V	F	F	V	V
F	V	F	F	F
F	F	F	V	V


Circuito 2

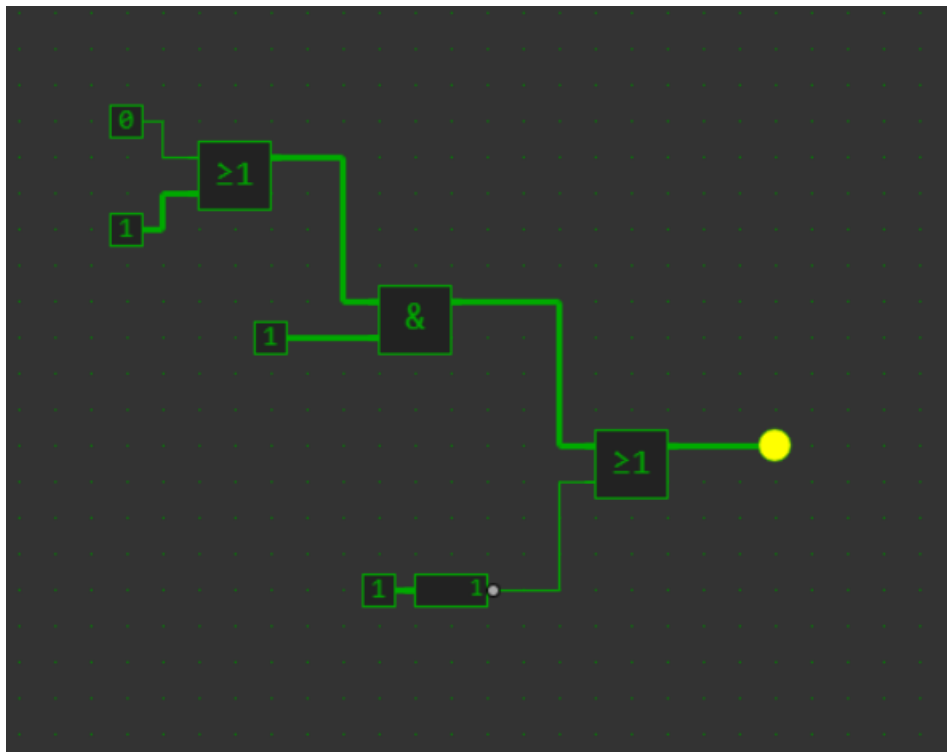

p q	p OR q	(p OR q) AND q	NOT q	[(p OR q) AND q] OR (NOT q)
V V	V	V	F	V
V F	V	F	V	V
F V	V	V	F	V
F F	F	F	V	V


Búsqueda

Circuito 3

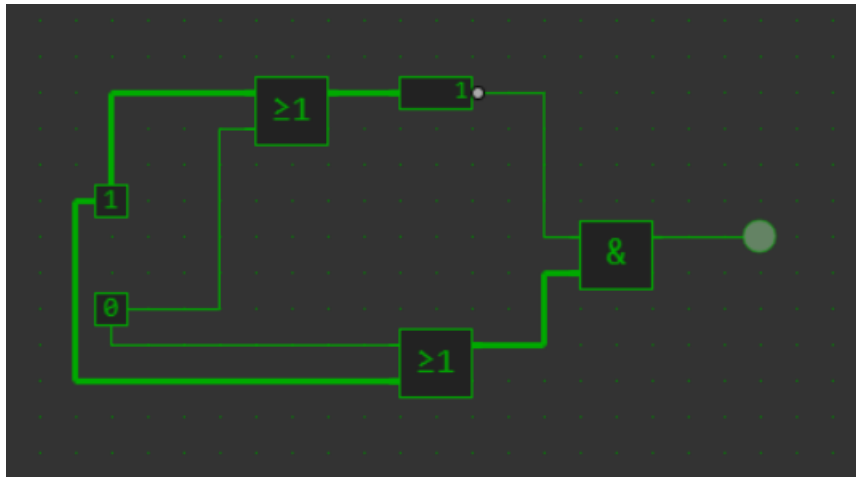

p	q	p OR q	NOT (p OR q)	NOT (p OR q) AND (p OR q)
V	V	V	F	F
V	F	V	F	F
F	V	V	F	F
F	F	F	V	F

Circuito 4

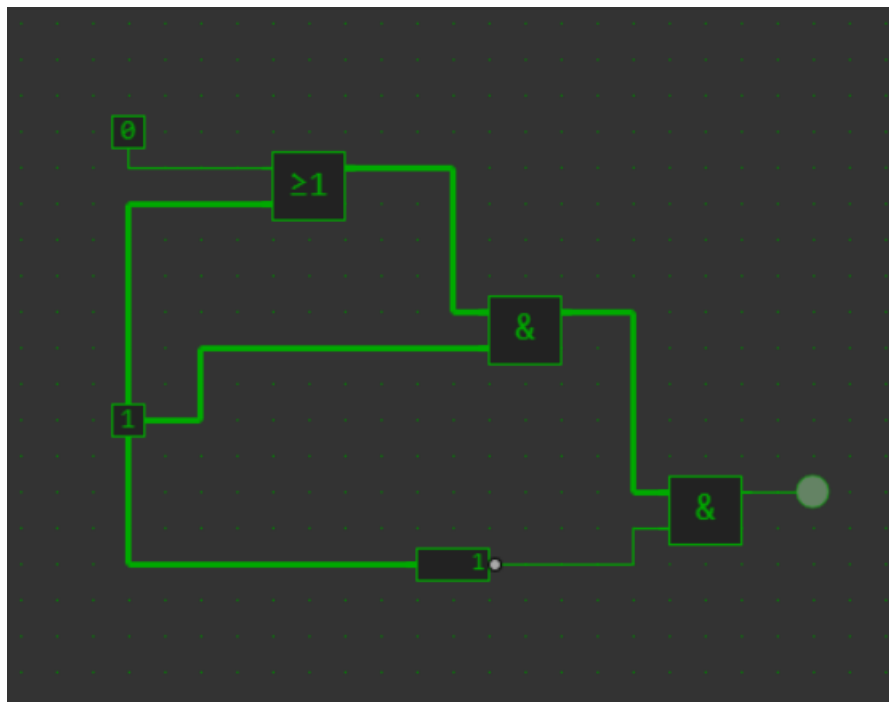

p q	p OR q	(p OR q) AND q	NOT q	[(p OR q) AND q] AND (NOT q)
V V	V	V	F	F
V F	V	F	V	F
F V	V	V	F	F
F F	F	F	V	F